

---

# EE230 RFIC II

Fall 2018


Project Description

Oct. 28, 2018

Sang-Soo Lee  
Electrical Engineering Department  
San Jose State University  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)

# Project Description

## 1.9 GHz Charge Pump PLL

 



# Project Logistics

---

1. A group of 2 students
2. Working alone is fine
3. Project presentation on Nov. 27, 29, and Dec. 4.
4. One Project Report per group
  - Report should include the followings
    - Verilog-A or Verilog-AMS model and simulation results
    - Matlab behavioral simulation showing stability
    - Schematic capture of major blocks
    - Key Simulation results
    - Summary table showing the performance achieved
  - Report should be in IEEE conference paper format
  - Project Report due : 5 PM, Dec 10

## Project Description

## Reference: Charge Pump PLL\*

  

\* A 216 $\mu$ W 281MHz-1.126GHz Self-Calibrated SSCG PLL  
with 0.6V Supply Voltage in 55nm DDC™ CMOS Process – Unpublished work by Ahn & Lee

# Target Spec – Beat the best

TABLE I  
PERFORMANCE COMPARISON

	Ref[4]	This Work	
Process	0.13 $\mu$ m CMOS	Conventional 55nm CMOS	DDC 55nm CMOS
Supply Voltage	0.5V	0.85V	0.6V
PLL Locking Range [MHz]	360 ~ 610	257 ~ 1,218	281 ~ 1,126
RMS Jitter	8.01ps @550MHz	12.75ps @800MHz	8.16ps @800MHz
Power Consumption	1.25mW @550MHz	701 $\mu$ W @800MHz	216 $\mu$ W @ 800MHz
Active Die Area	0.04mm <sup>2</sup>	0.06mm <sup>2</sup>	0.06mm <sup>2</sup>
FoM [dB]	-221	-219	-228

$$* \mathbf{FoM} = 10 \cdot \log \left( \text{Jitter}^2 \cdot \text{Power} / 1mW \right)$$

# Design Constraint


- Architecture: Type-II Integer-N Charge Pump PLL
- Goal is to achieve FoM < -220 dB with the following constraint
  - Use 45nm technology PDK in gpdk045
  - VDD=1V
  - Device types available for the design
  - → nmos1v, pmos1v, resnsppoly, Ideal cap
  - RefCLK = 30 MHz
  - Bias Current : Use “ideal\_bias” current cell in the next slide
  - PVT corners
    - TT, 1V, 27C
    - SS, FF
    - 0.9V, 1.1V
    - -40C, 125C

# Bias Current

Lib: ee288lib

Cell: ideal\_bias

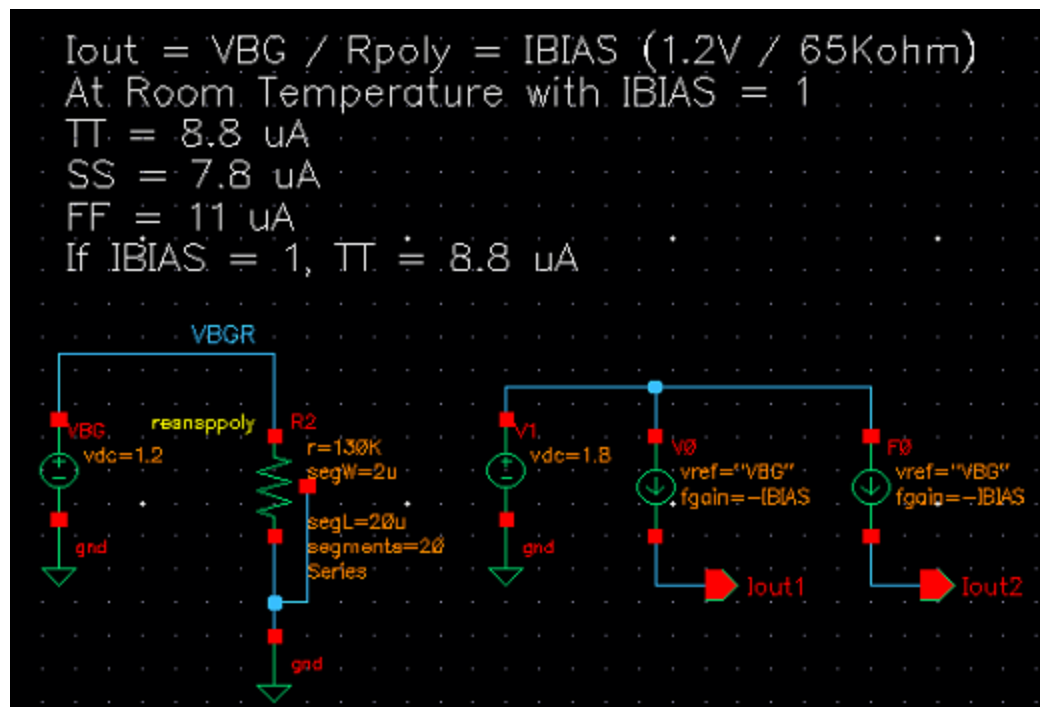Choose different value for IBIAS to vary the output current level



# References

---

## ➤ PLL

- Rishi Ratan, From Chapter 3, MS Thesis, UIUC, 2014
- H. Ahn and S. Lee, *File name: VLSI2014\_PLL\_v7*

## ➤ Verilog-A

- VCO\_VerilogA\_ECE546\_UIUC
- PLL\_Jitter\_measurement\_in\_Spectre

## ➤ Verilog-AMS

- Rishi Ratan, Chapter 6, MS Thesis, UIUC, 2014

## ➤ Jitter measurement

- PLL\_Jitter\_measurement\_in\_Spectre
- <https://www.youtube.com/watch?v=VvkHPoSVpVc>