

## EE230 – HW3 Report

### PLL System Design

(Using VerilogA & Matlab)

Muhammad Aldacher

Student ID: 011510317

#### 1. Schematic of the PLL system:

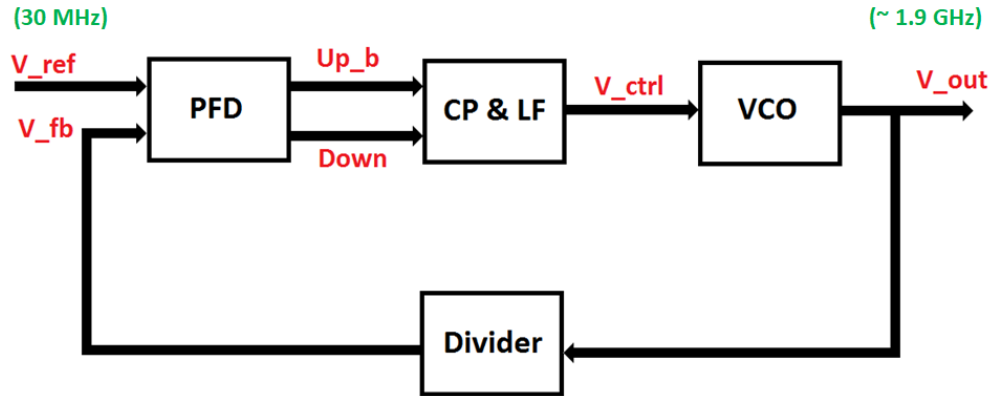


Fig. 1. PLL System Block Diagram


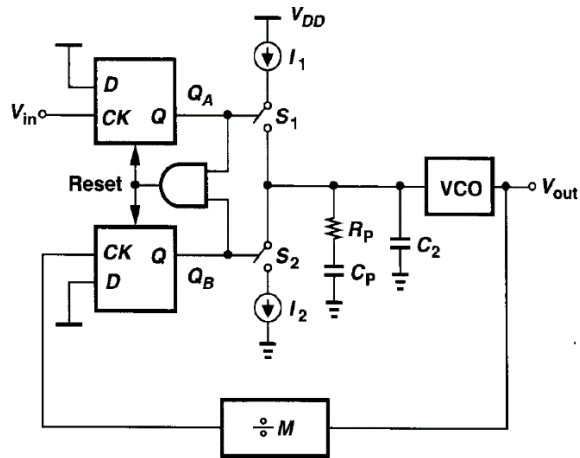


Fig. 2. Typical Charge Pump PLL System

Table 1. System Parameters Used

| Parameter     | Value          |
|---------------|----------------|
| $F_{REF}$     | 30 MHz         |
| $F_{OUT}$     | 1.9 GHz        |
| $M_{Divider}$ | 64             |
| $I_{CP}$      | 100 $\mu$ A    |
| $K_{VCO}$     | 600 MHz/V      |
| $R_P$         | 6.5 K $\Omega$ |
| $C_P$         | 100 pF         |
| $C_2$         | 10 pF          |

## 2. System Analysis:

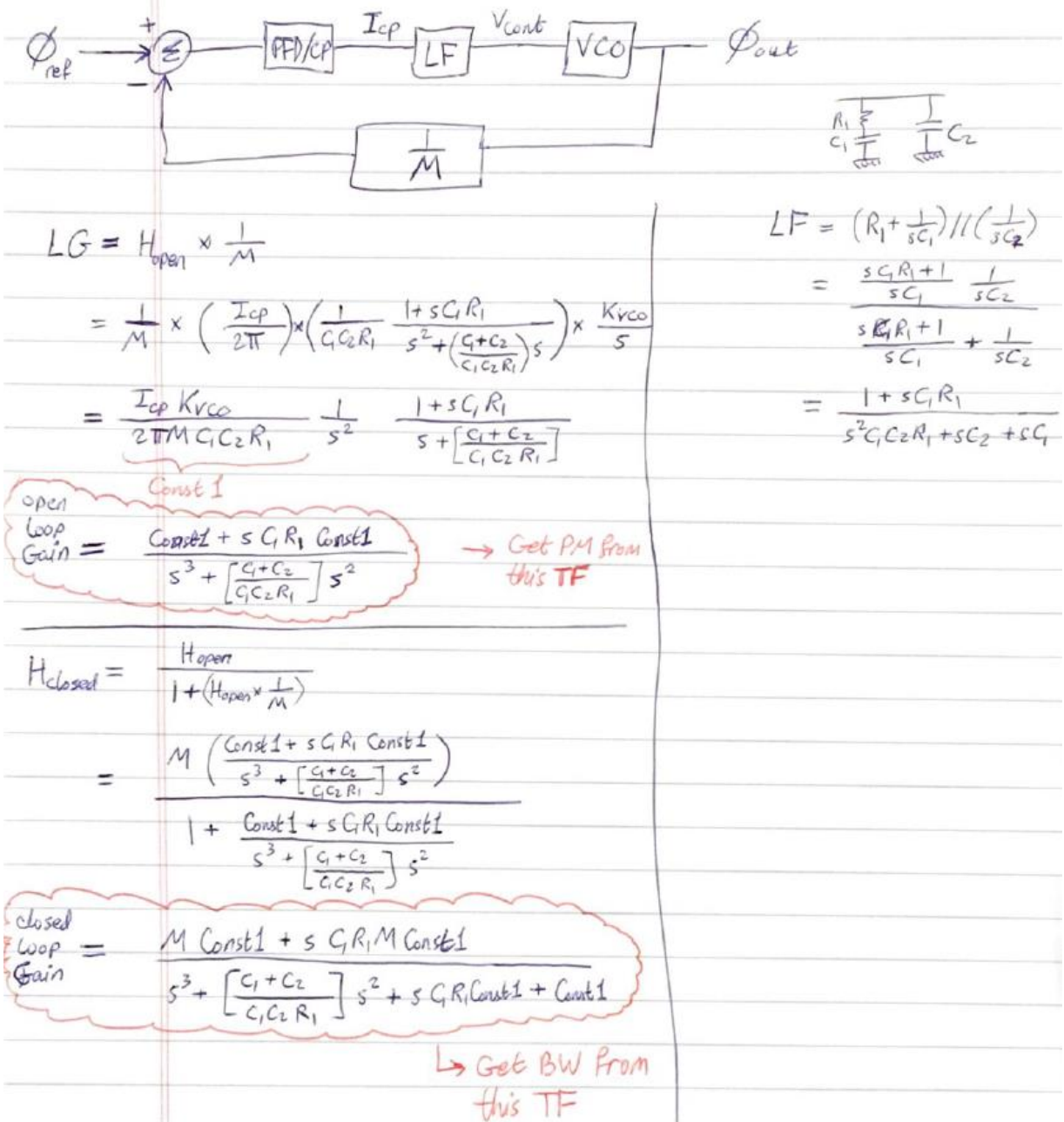


$$H_{\text{Open Loop Gain}}(s) = \frac{I_{cp} K_{VCO}}{2\pi N} \frac{s R_1 C_1 + 1}{s^2 (s R_1 C_1 C_2 + (C_1 + C_2))}$$


$$H_{\text{Closed Loop Gain}}(s) = \frac{I_{cp} K_{VCO}}{2\pi} \frac{s R_1 C_1 + 1}{s^3 R_1 C_1 C_2 + s^2 (C_1 + C_2) + s R_1 C_1 \frac{I_{cp} K_{VCO}}{2\pi N} + \frac{I_{cp} K_{VCO}}{2\pi N}}$$

### 3. System Stability (Matlab):

#### 3.1 Bode Plots:

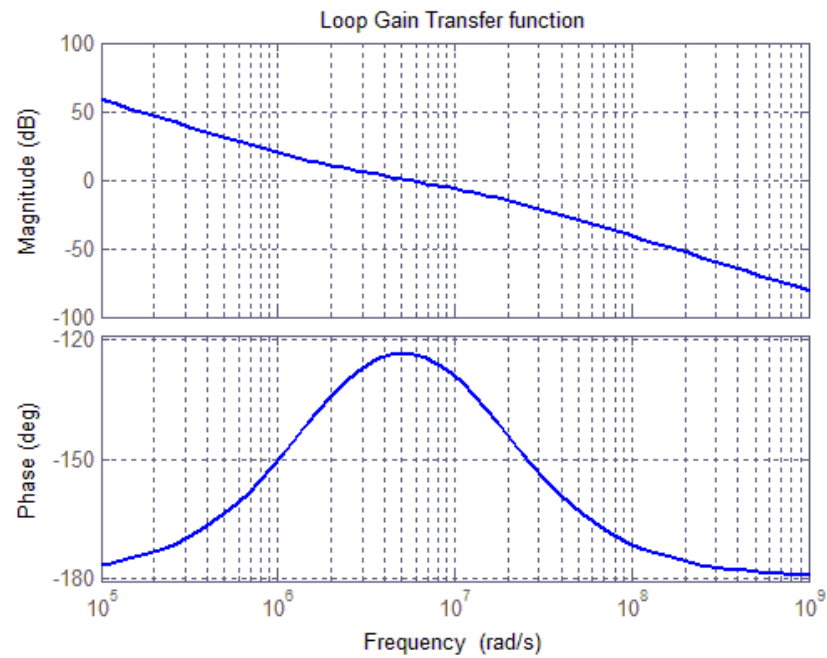

**Fig. 3. Open-Loop Bode Plots**

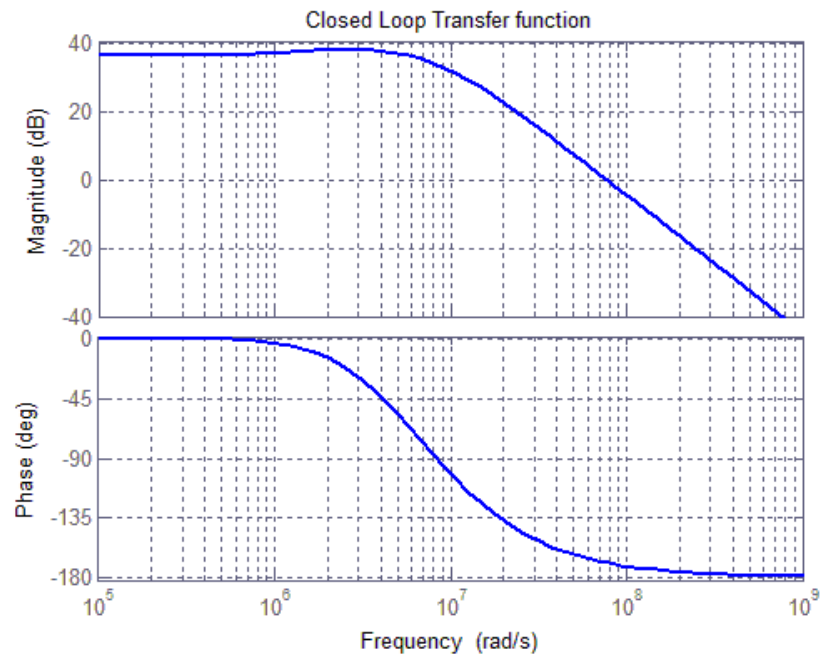

**Fig. 4. Closed-Loop Bode Plots**

Table 2. Open-Loop &amp; Closed-Loop Parameters

| Parameter        |            | Value     |
|------------------|------------|-----------|
| Zero             | $f_z$      | 0.245 MHz |
| Unity-Gain BW    | $f_{ugb}$  | 0.871 MHz |
| Pole             | $f_{p3}$   | 2.693 MHz |
| Max Phase Margin | $PM_{Max}$ | 56.44°    |
| Phase Margin     | PM         | 56.38°    |
| Closed-Loop BW   | BW         | 1.41 MHz  |

### 3.2 Code:

```

clc; close all;
figure
Icp = 100e-6;      Kvco = 2*pi*600e6;      M = 64;
R1 = 6.5e3;        C1 = 100e-12;          C2 = C1/10;
%-----
% Open Loop Gain:
wz = 1 / (R1*C1)
w_ugb = wz * sqrt((C1/C2)+1);
wp3 = (C1 + C2) / (R1*C1*C2);
PM_Max = (atan(w_ugb/wz) - atan(w_ugb/wp3)) * 360 / (2*pi)
Const1 = (Icp*Kvco) / (2*pi*M*C1*C2*R1);

H = tf([C1*R1*Const1 Const1],[1 ((C1+C2)/(C1*C2*R1)) 0 0]);
bode(H)
[Gm,Pm,Wgm,Wpm] = margin(H);
Pm
hold on; grid on; title('Loop Gain Transfer function')
set(findall(gcf,'type','line'),'linewidth',2)
%-----
% To find the zero & pole accurately:
b = [C1*R1*Const1 Const1];
a = [1 ((C1+C2)/(C1*C2*R1)) 0 0];
fvtool(b,a,'polezero')
[b,a] = eqtflength(b,a);
[z,p,k] = tf2zp(b,a)           %<-- z = zero, p = pole

gain = db2mag(0);
wc = getGainCrossover(H,gain)   %<-- wc = unity-gain BW
%-----
% Closed Loop Gain:
figure
H = tf([(C1*R1*Const1*M) (M*Const1)],[1 ((C1+C2)/(C1*C2*R1)) (C1*R1*Const1) Const1]);
bode(H)
[Gm,Pm,Wgm,Wpm] = margin(H);

BW = (bandwidth(H))/(2*pi)
fz = wz / (2*pi)
fp = wp3 / (2*pi)
fc = wc / (2*pi)
hold on; grid on; title('Closed Loop Transfer function')
set(findall(gcf,'type','line'),'linewidth',2)

```

#### 4. System Simulations:

##### 4.1 Open-Loop Test Bench:

 


Fig. 5. Test Bench for PFD, CP, LF, & VCO in an Open Loop

 


Fig. 6. Waveforms when Feedback signal is leading (with respect to Reference)



Fig. 7. Waveforms when Feedback signal is lagging (with respect to Reference)

4.2 VCO & Divider Test Bench:

 


Fig. 8. Test Bench for VCO & Divider

 


Fig. 9. Output Waveforms of VCO & Divider

4.3 Whole PLL Test Bench:


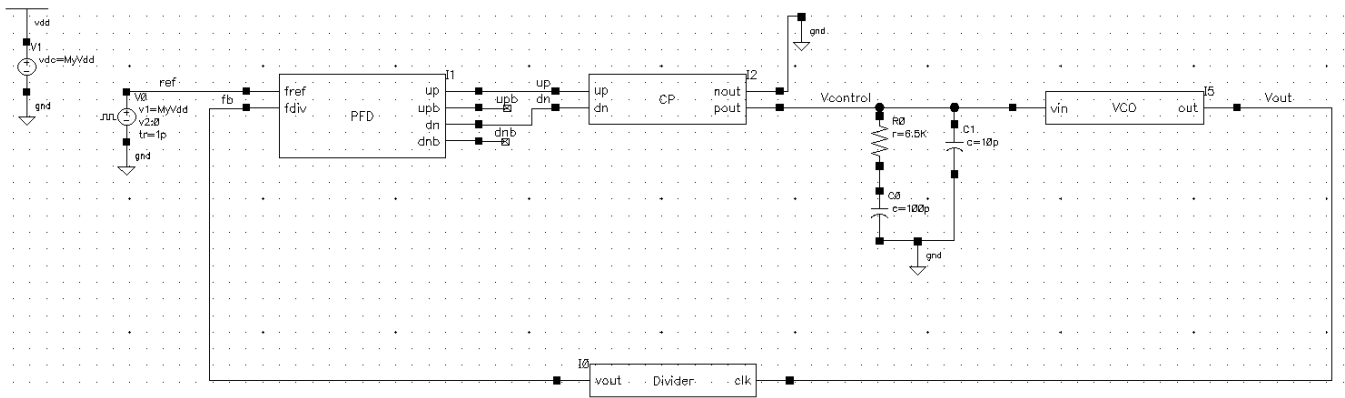


Fig. 10. Test Bench for the Whole PLL System

 

**Fig. 11. Output Waveforms of the PLL when locking**

## 5. VerilogA codes:

### 5.1 PFD code:

```
// VerilogA for EE230_PLL_VerilogA, PFD, verilogA
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module PFD(up,dn,upb,dnb,fref,fdiv);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
input fref;
```

```
input fdiv;
```

```
output up,upb,dn,dnb;
```

```
electrical fref,fdiv,up,upb,dn,dnb;
```

```
real fv_rst, fr_rst, reset, upr,upbr,dnr,dnbr;
```

```
analog begin
```

```
    @(cross(V(fref) - clk_threshold, +1))
```

```
    begin
```

```
        upr = 1; upbr = 0; end
```

```
    @(cross(V(fdiv) - clk_threshold, +1))
```

```
    begin
```

```
        dnr = 1; dnbr = 0; end
```

```

        if(dnr == upr) begin
            upr = 0; dnr = 0; upbr = 1; dnbr = 1; end

        V(up) <+ transition(upr,delay,ttime);      V(dn) <+ transition(dnr,delay,ttime);
        V(upb) <+ transition(upbr,delay,ttime);    V(dnb) <+ transition(dnbr,delay,ttime);
    end
endmodule

```

## 5.2 Charge Pump code:

```

// VerilogA for EE230_PLL_VerilogA, CP, verilogA
`include "constants.vams"
`include "disciplines.vams"

module CP(pout,nout,up,dn);
    parameter real cur = 100u; //output current 100uA
    parameter real threshold=0.5;
    input up, dn;
    output pout, nout;
    electrical pout, nout, up, dn;
    real out;

    analog begin
        @(initial_step) out = 0.5;

        if((V(dn)>0.5) && (V(up)<0.5)) begin
            out = -cur; end
        else if((V(dn)<0.5) && (V(up)>0.5)) begin
            out = cur; end
        else out = 0.0;

        I(pout, nout) <+ -transition(out, 0.0, 10n, 10n);
    end
endmodule

```

## 5.3 VCO code:

```

// VerilogA for testlib, VCO, VerilogA
`include "constants.vams"
`include "disciplines.vams"

module VCO ( vin , out ) ;

    input vin ; output out ;
    electrical vin ; electrical out ;

```



```

parameter real Vmin=0; // Minimum input voltage
parameter real Vmax=Vmin+1 from (Vmin : inf) ; // Maximum input voltage
parameter real Fmin= 1.6e9 from ( 0 : inf) ; // Minimum output frequency
parameter real Fmax=2.2e9 from (Fmin : inf) ; // Maximum output frequency
parameter real Vamp = 1 from [ 0 : inf) ; // Output sinusoid amplitude
parameter real ttol=1u/Fmax from ( 0 : 1 /Fmax ) ; // Crossing time tolerance
parameter real vtol = 1e-9; // Voltage

parameter integer min_pts_update=32 from [ 2 : inf) ;

parameter real tran_time = 10e-12 from ( 0 : 0.3 /Fmax ) ;
parameter real jitter_std_ui = 0 from [ 0 : 1 ) ;

// Internal Variables
real freq, phase, jitter_rad, dPhase, phase_ideal;
integer n ;
integer seed ;

analog begin
    @( initial_step )
    begin
        seed = 671;
        n = 0 ;
        dPhase = 0 ;
        jitter_rad = jitter_std_ui * 2 * `M_PI ;
    end

    // compute the freq from the input voltage
    freq = ( (V(vin) - Vmin) * (Fmax - Fmin) / (Vmax - Vmin) ) + Fmin ;

    $bound_step (1/( min_pts_update * freq ) ) ;
    if ( freq > Fmax) freq = Fmax ;
    if ( freq < Fmin) freq = Fmin ;
    phase_ideal = 2 * `M_PI * idtmod(freq, 0.0, 1.0, -0.5);
    phase = phase_ideal + dPhase ;

    @( cross(phase_ideal + `M_PI/2, +1, ttol, vtol) or cross(phase_ideal - `M_PI/2, +1, ttol, vtol))
    begin
        dPhase = $rdist_normal(seed,0,jitter_rad); end

    @( cross(phase + `M_PI/2, +1, ttol, vtol) or cross(phase - `M_PI/2, +1, ttol, vtol))
    begin
        n = ( phase >= -`M_PI/2)&&(phase < `M_PI / 2 ) ; end

    // generate the output
    V( out ) <+ transition (n?Vamp:0 , 0 , tran_time);

```

```
end
endmodule
```

#### **5.4 Divider code:**

```
// VerilogA for EE230_PLL_VerilogA, Divider, veriloga
`include "constants.vams"
`include "disciplines.vams"

module Divider(clk,vout);

parameter real vtrans=0.5;
parameter real delay = 0;
parameter real ttime = 1p;
parameter real clk_threshold = 0.5;
parameter real N = 64;

input clk; output vout;
electrical clk,vout;
real counter,v_out;

analog begin

    @(initial_step) begin
        v_out = 0; counter = 0; end

    @(cross(V(clk) - clk_threshold, +1))
    begin
        if(counter < ((N/2)-1)) begin
            counter = counter +1; v_out = 0; end
        else if(counter < (N-1)) begin
            counter = counter +1; v_out = 1; end
        else if (counter == (N-1)) begin
            counter = 0; v_out = 0; end
    end

    V(vout) <+ transition(v_out,delay,ttime);

end
endmodule
```