

# ECEN620: Network Theory Broadband Circuit Design Fall 2018

---

## Lecture 6: Loop Filter Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---


- HW2 is due Oct 11
  - Requires transistor-level design
  - For 90nm CMOS device models, see [http://www.ece.tamu.edu/~spalermo/ecen689/cadence\\_90nm.pdf](http://www.ece.tamu.edu/~spalermo/ecen689/cadence_90nm.pdf)
  - Can use other technology models if they are a 130nm or more advanced CMOS node

# Agenda

---



- Loop filter circuits
  - Voltage-mode filters
  - Charge-Pump PLL PI filter
  - Filter with capacitive multiplier
  - Split Proportional & Integral Path Filters
  - Pattern Jitter
  - Sample-Reset Loop Filter
- Some loop filter papers are posted on the website

# PLL Block Diagram

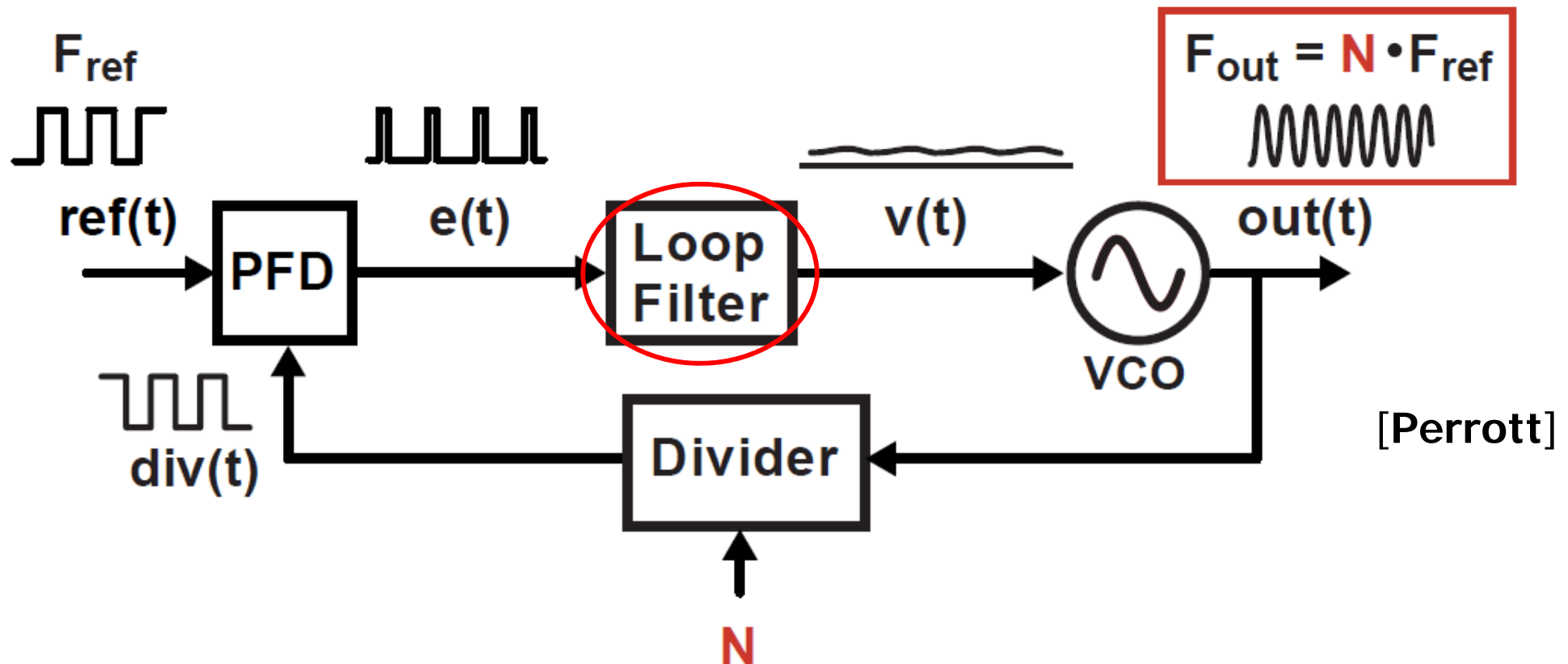

- The lowpass loop filter extracts the average of the phase detector error pulses in order to produce the VCO control voltage

# Passive Lag-Lead Filter

  


$$F(s) = \frac{1 + s\tau_2}{1 + s(\tau_1 + \tau_2)}$$

$$\tau_1 = R_1C \quad \tau_2 = R_2C$$

- Dimensionless voltage-mode filter used in Type-1 PLLs
- Called lag-lead because the pole is at a lower frequency than the zero
- Ideally, the passive filter displays no nonlinearity

# Active Lag-Lead Filter

 


$$F(s) = K_a \frac{1 + s\tau_2}{1 + s\tau_1}$$

$$\tau_1 = R_1 C \quad \tau_2 = R_2 C \quad K_a = -\frac{C_1}{C_2}$$

- Dimensionless voltage-mode filter used in Type-1 PLLs
- Active filter allows for potential gain in the loop filter
- Opamp noise and linearity can impact PLL performance
 
# Active Proportional-Integral (PI) Filter



$$F(s) = -\frac{1 + s\tau_2}{s\tau_1}$$

$$\tau_1 = R_1 C \quad \tau_2 = R_2 C$$

- Dimensionless voltage-mode filter used in Type-2 PLLs
- Opamp noise and linearity can impact PLL performance
- Opamp open loop gain limits the low-frequency gain and ideal transfer function

# Closed-Loop Transfer Functions

Passive Lag - Lead Filter

$$F(s) = \frac{1 + s\tau_2}{1 + s(\tau_1 + \tau_2)} \rightarrow H(s) = \frac{\frac{K_{PD}K_{VCO}\tau_2}{\tau_1 + \tau_2} \left( s + \frac{1}{\tau_2} \right)}{s^2 + \left( \frac{1 + K_{PD}K_{VCO}\tau_2/N}{\tau_1 + \tau_2} \right) s + \frac{K_{PD}K_{VCO}}{N(\tau_1 + \tau_2)}}$$

$$\omega_n = \sqrt{\frac{K_{PD}K_{VCO}}{N(\tau_1 + \tau_2)}} \quad \zeta = \frac{\omega_n}{2} \left( \tau_2 + \frac{N}{K_{PD}K_{VCO}} \right)$$

Active Lag - Lead Filter (Assuming Overall Negative Feedback)

$$F(s) = K_a \frac{1 + s\tau_2}{1 + s\tau_1} \rightarrow H(s) = \frac{\frac{K_{PD}K_aK_{VCO}\tau_2}{\tau_1} \left( s + \frac{1}{\tau_2} \right)}{s^2 + \left( \frac{1 + K_{PD}K_aK_{VCO}\tau_2/N}{\tau_1} \right) s + \frac{K_{PD}K_aK_{VCO}}{N\tau_1}}$$

$$\omega_n = \sqrt{\frac{K_{PD}K_aK_{VCO}}{N\tau_1}} \quad \zeta = \frac{\omega_n}{2} \left( \tau_2 + \frac{N}{K_{PD}K_aK_{VCO}} \right)$$


Active PI Filter (Assuming Overall Negative Feedback)

$$F(s) = -\frac{1 + s\tau_2}{s\tau_1} \rightarrow H(s) = \frac{\frac{K_{PD}K_{VCO}\tau_2}{\tau_1} \left( s + \frac{1}{\tau_2} \right)}{s^2 + \left( \frac{K_{PD}K_{VCO}\tau_2}{N\tau_1} \right) s + \frac{K_{PD}K_{VCO}}{N\tau_1}}$$

$$\omega_n = \sqrt{\frac{K_{PD}K_{VCO}}{N\tau_1}} \quad \zeta = \frac{\omega_n}{2} \tau_2$$




# Charge Pump PLL Passive PI Loop Filter

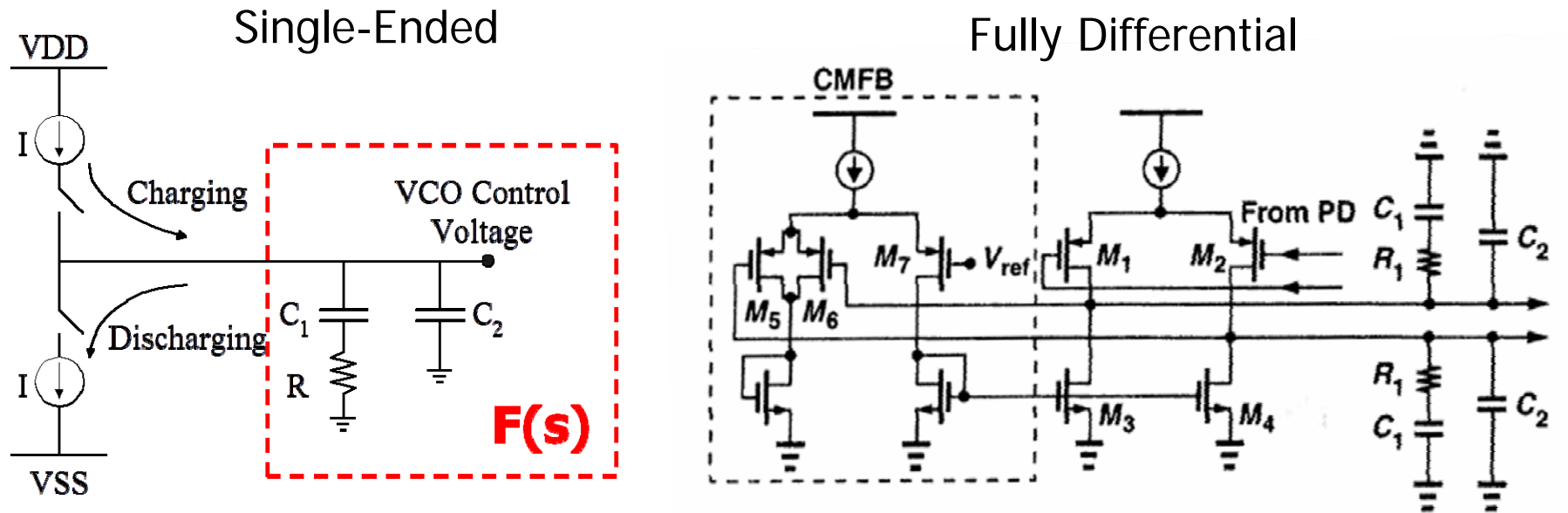


- Simple passive filter is most commonly used
- Integrates low-frequency phase errors onto C1 to set average frequency
- Resistor (proportional gain) isolates phase correction from frequency correction
- Primary capacitor C1 affects PLL bandwidth
- Zero frequency affects PLL stability
- Resistor adds thermal noise which is band-pass filtered by PLL

# Loop Filter Transfer Function

- Neglecting secondary capacitor,  $C_2$

 

 
$$F(s) = \frac{V_c(s)}{I_e(s)} = \frac{R \left( s + \frac{1}{RC_1} \right)}{s}$$




# Loop Filter Transfer Function

- With secondary capacitor,  $C_2$

 

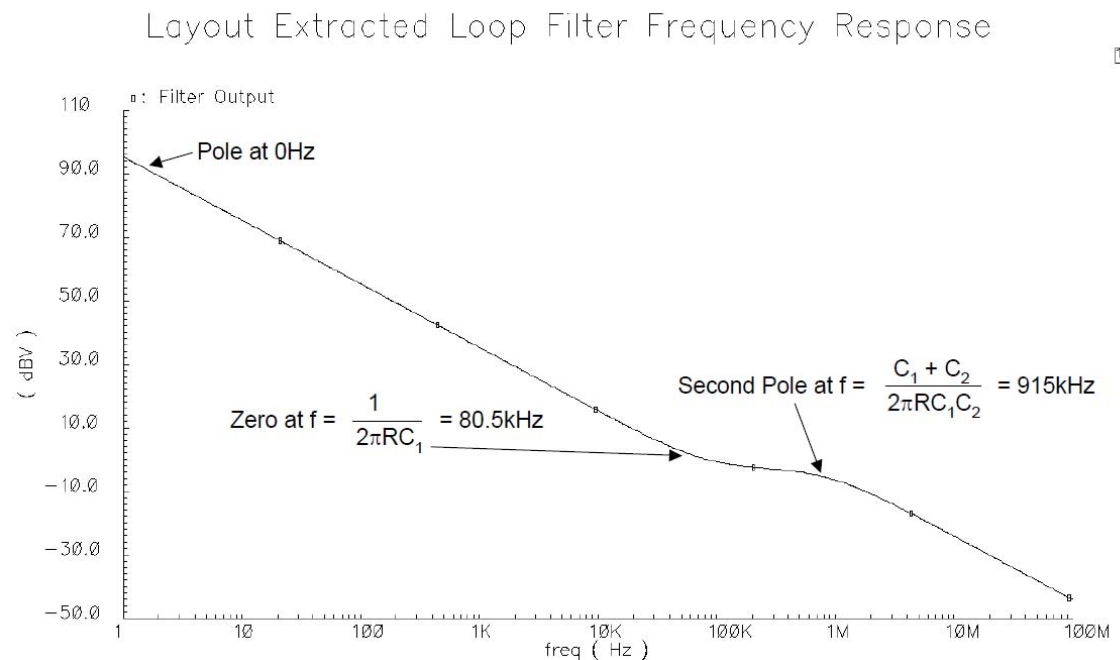
$$Z(s) = \frac{\frac{1}{C_2} \left( s + \frac{1}{RC_1} \right)}{s^2 + \frac{s(C_1 + C_2)}{RC_1 C_2}}$$




# Why have $C_2$ ?

- Secondary capacitor smoothes control voltage ripple
- Can't make too big or loop will go unstable
  - $C_2 < C_1/10$  for stability
  - $C_2 > C_1/50$  for low jitter

PLL Synthesizing a 380MHz Signal

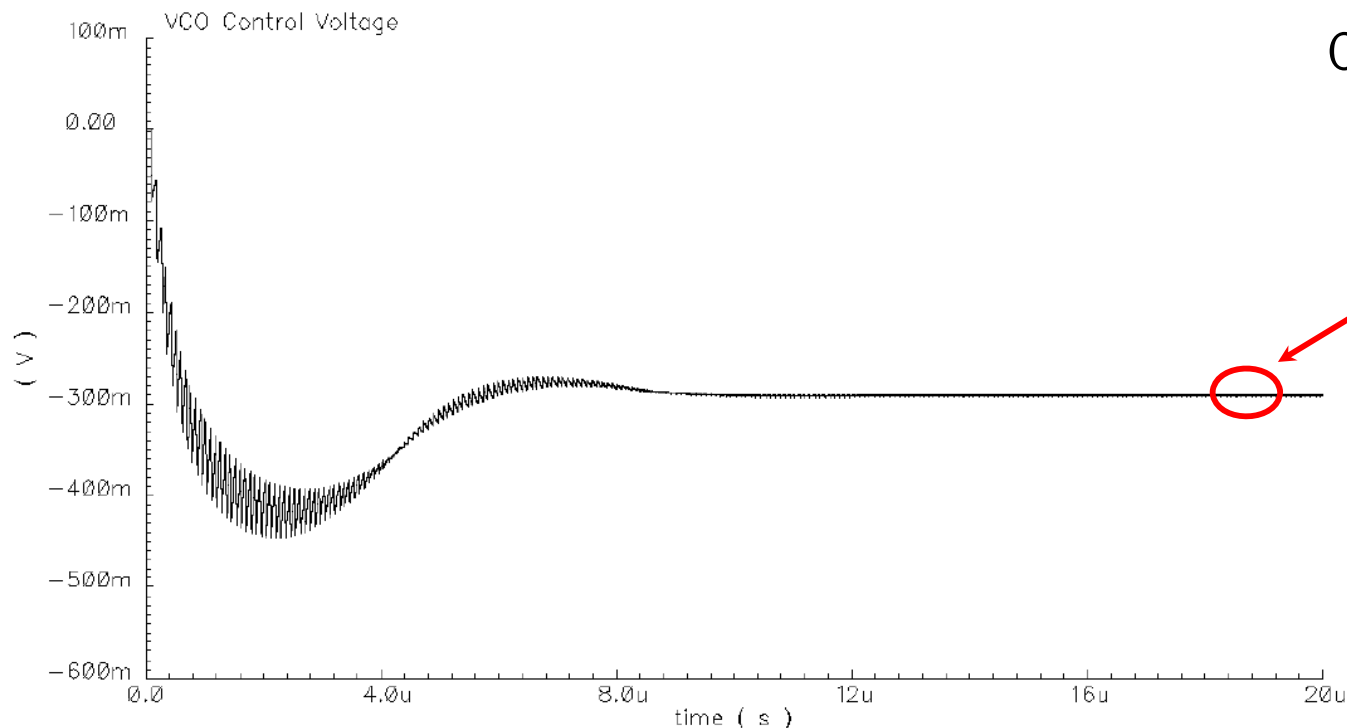


Control Voltage Ripple

 
 
# Loop Filter Resistors

---


- Poly, diffusion, and N-well resistors are commonly used
- MOSFET resistors can be used if the resistor is placed “below” the C1 cap
  - This ensures a constant  $V_{GS}$  voltage on the transistor
- Programmable R value possible with switches
  - Switches should be CMOS transmission gates to minimize parasitic switch resistance variation with control voltage level
  - Good practice is to make  $R_{switch} < 10\%$  of the main filter R to minimize the impact of switch resistance variations


 
# R or C on Top?

---

- Ideally, the loop filter has the same transfer function and transient response independent of the RC order
- In reality, the bottom-plate capacitance and switch resistance variation will impact this ideal transfer function
- If the cap is on top, the bottom-plate capacitance will introduce another high frequency pole
- If the resistor is on top, any switch resistance will have increased variation with the control voltage level




# Loop Filter Capacitors

---

- To minimize area, we would like to use highest density caps
- Thin oxide MOS cap gate leakage can be an issue
  - Similar to adding a non-linear parallel resistor to the capacitor
  - Leakage is voltage and temperature dependent
  - Will result in excess phase noise and spurs
- Metal caps or thick oxide caps are a better choice
  - Trade-off is area
- Metal cap density can be  $< 1/10$  thin oxide caps
- Filter cap frequency response can be relatively low, as PLL loop bandwidths are typically 1-50MHz

# Third-Order Loop Filter


 


[Shu JSSC 2003]

The 160pF capacitance in TSMC 0.35um CMOS takes about  $0.2\text{mm}^2$ . To reduce its area, it is implemented via a 10pF capacitor scaled up by a factor of 16.



# Capacitor Multiplier

  


Current ratio  $M=15$

Capacitance  $\times 16$
 
# Capacitor Multiplier Transfer Function

$$y_{in} = \frac{i_{in}}{v_{in}} = g_{oA} + s \left[ C_{p2} + (M + 1)C_i \frac{1 + s \frac{C_{p1}}{(M+1)g_{m1}}}{1 + s \frac{C_i + C_{p1}}{g_{m1}}} \right]. \quad (7)$$



Looking at the impedance, we get 2 poles and a zero  
 $\omega_{c1}$  and  $\omega_{c3}$  are poles,  $\omega_{c2}$  is a zero

Low freq. pole  
 (ideally at 0)

High freq. zero  
 (ideally at  $\infty$ )

High freq. pole  
 (ideally at  $\infty$ )

$$\omega_{c1} = \frac{g_{oA}}{C_{p2} + (M + 1)C_i} \approx \frac{g_{oA}}{C_1}$$


$$\omega_{c2} = \frac{g_{m1}}{(C_i + C_{p1})} \approx \frac{(M + 1)g_{m1}}{C_1}$$

$$\omega_{c3} = \frac{(M + 1)g_{m1}}{C_{p1}}.$$


Current ratio  $M=15$

Capacitance  $\times 16$


Original Filter

 

# Capacitance Multiplier Impedance

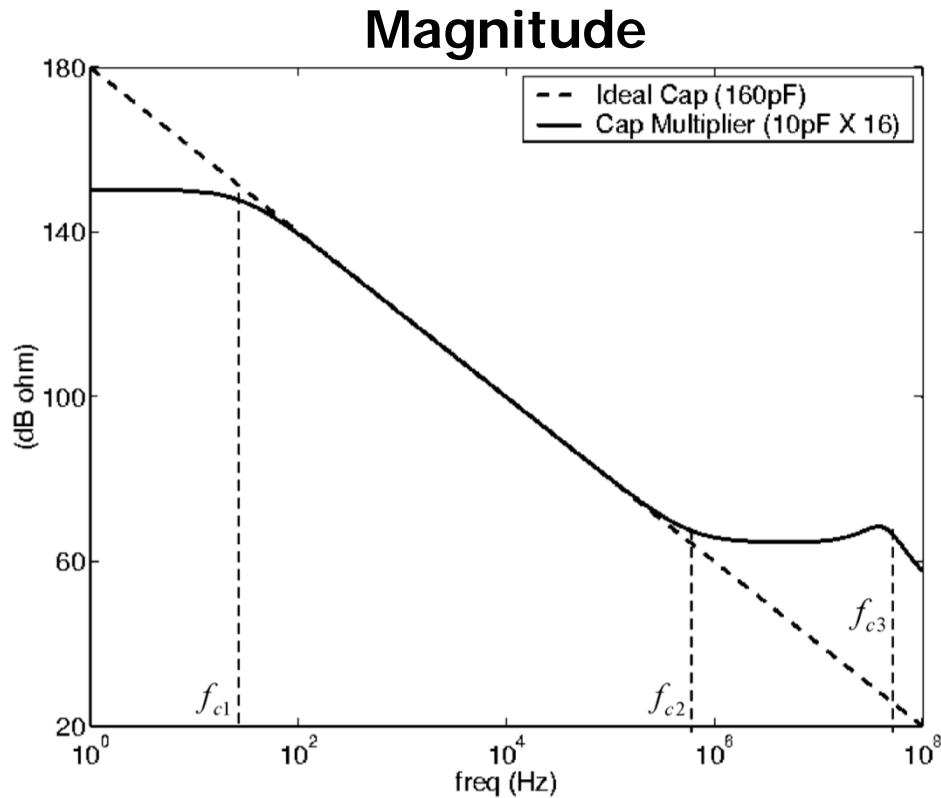

(a)

 


(b)

$$\omega_{c1} = \frac{g_{oA}}{C_{p2} + (M+1)C_i} \approx \frac{g_{oA}}{C_1} \quad (\text{dominant pole})$$

$$\omega_{c2} = \frac{g_{m1}}{(C_i + C_{p1})} \approx \frac{(M+1)g_{m1}}{C_1} \quad (\text{high frequency zero})$$

$$\omega_{c3} = \frac{(M+1)g_{m1}}{C_{p1}} \quad (\text{high frequency pole})$$
 
# Loop Filter Sim. w/ Capacitance Multiplier




(a) magnitude

(b) phase

- It shows that with capacitance scaling the large capacitor in the loop filter can be easily integrated on chip within small area
- This approach is simple and the leakage is very small

# Loop Filter Transfer Function


- Neglecting secondary capacitor,  $C_2$

 

$$F(s) = \frac{V_c(s)}{I_e(s)} = \frac{R \left( s + \frac{1}{RC_1} \right)}{s} = R + \frac{1}{sC_1}$$


Proportional term

Integral term

 


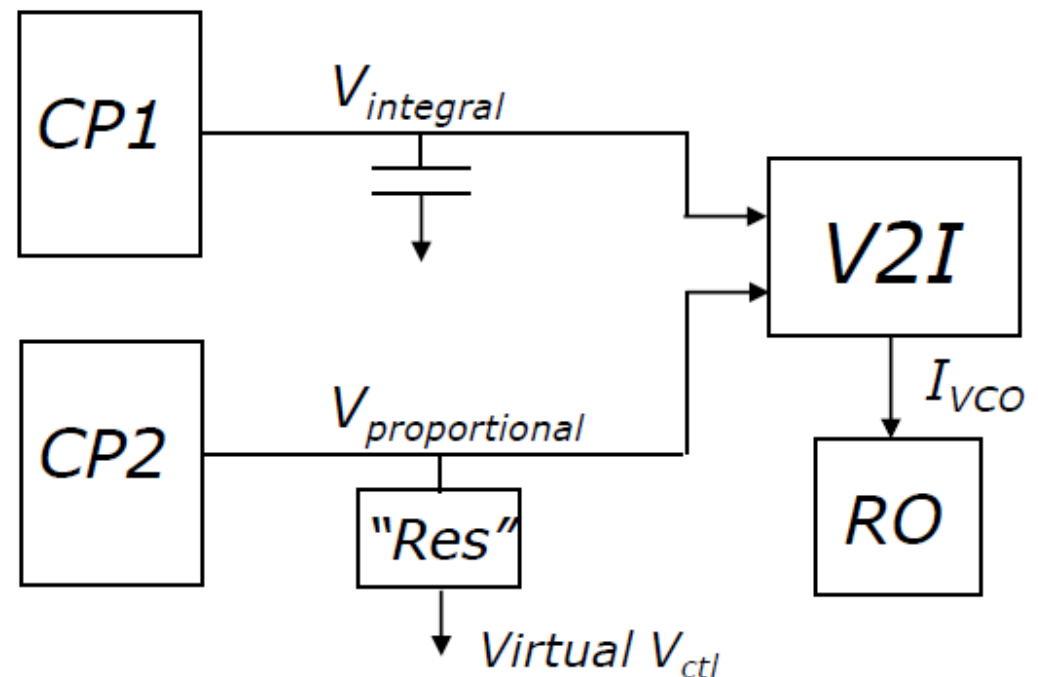
# Split Proportional & Integral Gain Path

- Proportional and integral gain paths can be split by utilizing 2 independent charge pumps driving the integral capacitor and the proportional effective resistor
- Often, the proportional and integral voltages are summed with a voltage-to-current converter to control a current-controlled oscillator (ICO)
  - Allows for self-biased PLL architectures whose normalized loop bandwidth and damping factor remains constant over different output frequencies
  - We will look at these PLL architectures in more detail later




# Control Voltage Ripple

PLL Synthesizing a 380MHz Signal

  

- After phase locking, disturbances at a time interval equal to the reference clock period cause time-domain period jitter and frequency-domain reference clock spurs
- Caused by charge pump current imbalance, loop filter leakage, and reference clock jitter


# Pattern Jitter

 

- A dominant form of pattern jitter is due to the proportional gain term,  $I_{CP} * R$
- Every time the reference clock goes high, charge pump mismatch current dropped on the filter resistor causes control voltage ripple
- This results in shorter (or longer) output cycles that occur at a time interval equal to the reference clock period




# Pattern Jitter w/ Secondary Capacitor

 

- Adding a secondary loop filter capacitor introduces extra filtering, which reduces the control voltage disturbance amplitude, but extends it over many cycles
- Makes an ideal second-order PLL into a third-order system
- Stability limits the size of  $C_2$
- Can we get this same effect without compromising stability?



 
# Sample-Reset Loop Filter w/ Single Capacitor




- A single-capacitor implementation still has a (reduced) ripple component due to the sample, hold, and reset operation
- Also, a very short reset pulse needs to be generated, which may be difficult to realize with the control logic

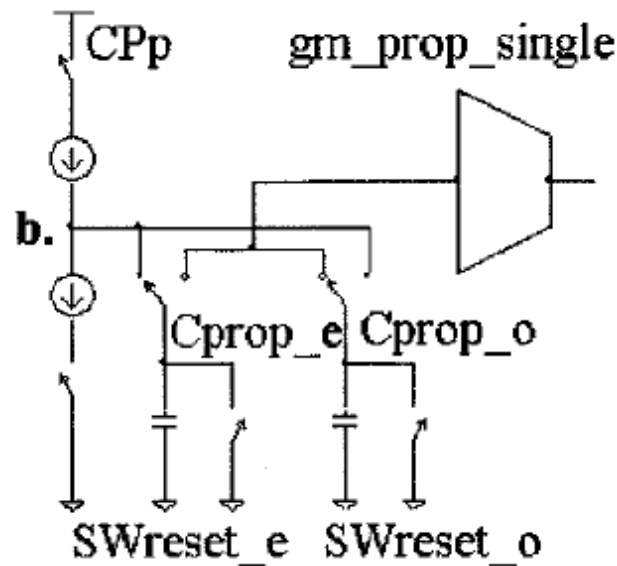
# Sample-Reset Loop Filter w/ Double Capacitors



 - With a double-capacitor implementation, the remaining ripple is dramatically reduced
- While one capacitor is being reset and then having the phase error sampled, the other capacitor which holds the previous sampled proportional voltage is attached to the gm output stage



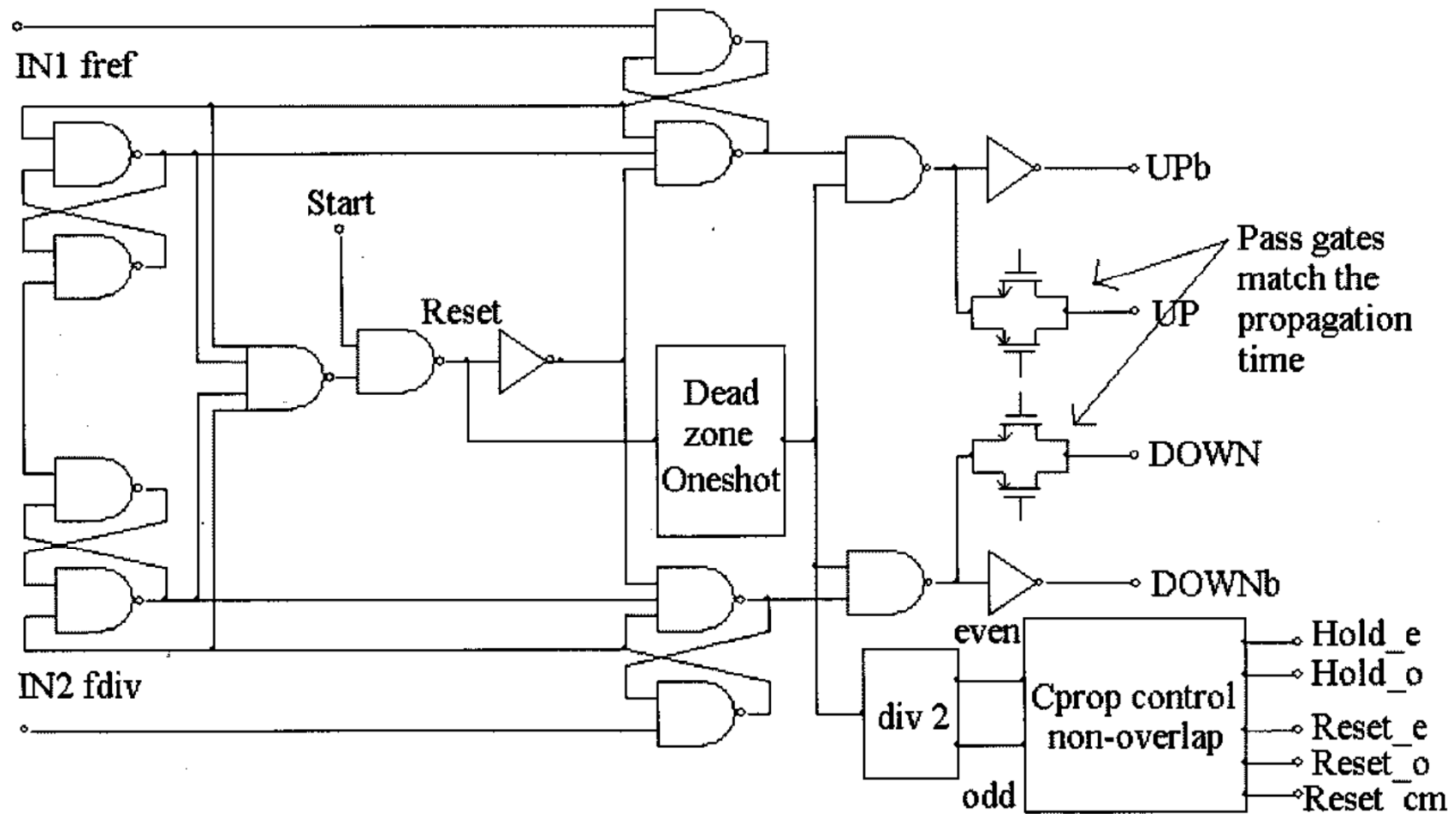
# Sample-Reset PLL PFD & Filter Switch Signal Generation



- The PFD reset signal is divided by 2 to produce the even and odd switch control signals
- During reset, the charge pump shouldn't be conducting and the filter capacitor can be applied to the main loop

# Sample-Reset PLL Small-Signal Model

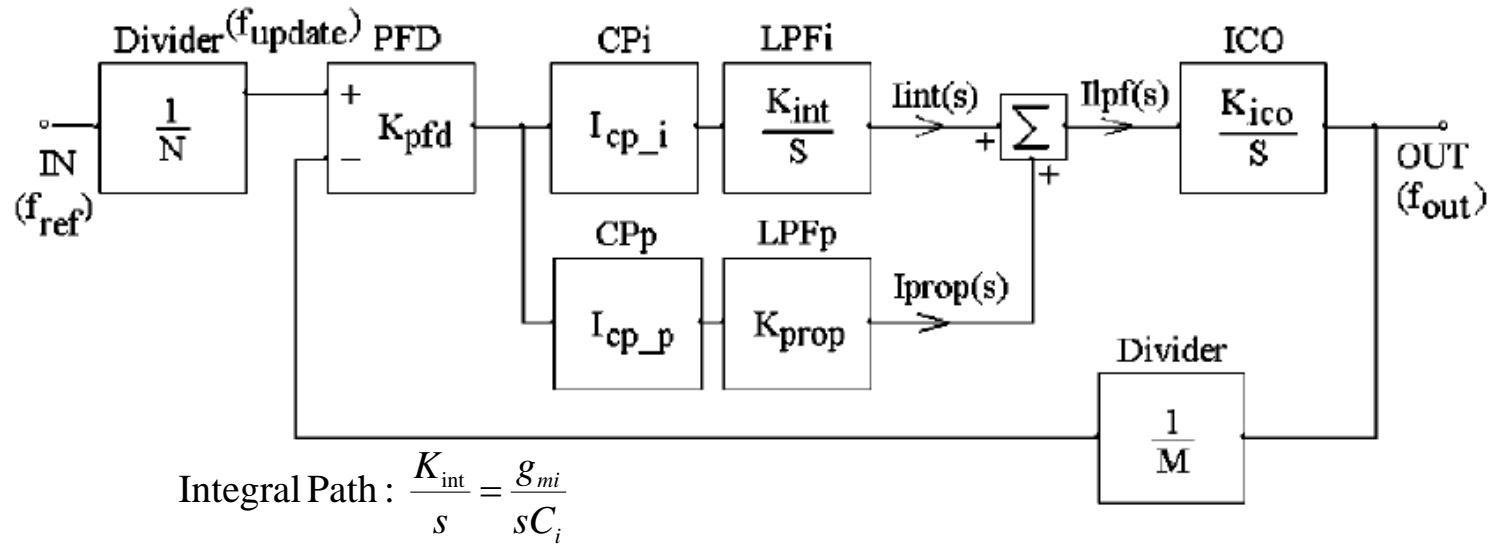

$$\text{Proportional Path : } K_{prop} = \frac{T_{update} g_{mp}}{C_p}$$

$$\text{Total ICO Current : } I_{lpf}(s) = I_{int}(s) + I_{prop}(s) = \left( \frac{I_{cp-i}}{2\pi} \right) \left( \frac{g_{mi}}{sC_i} \right) + \left( \frac{I_{cp-p}}{2\pi} \right) \left( \frac{T_{update} g_{mp}}{C_p} \right)$$


$$H(s) = \frac{\left( \frac{I_{cp-i}}{2\pi} \right) \left( \frac{g_{mi}}{C_i} \right) K_{ico} \left( 1 + s \left( \frac{I_{cp-p}}{I_{cp-i}} \right) \left( \frac{C_i}{C_p} \right) \left( \frac{T_{update} g_{mp}}{g_{mi}} \right) \right)}{s^2 + \left( \frac{I_{cp-p}}{2\pi} \right) K_{ico} T_{update} g_{mp} s + \frac{I_{cp-i} g_{mi} K_{ico}}{2\pi M C_i}}$$

$$\omega_n = \sqrt{\frac{I_{cp-i} g_{mi} K_{ico}}{2\pi M C_i}} \quad \omega_z = \left( \frac{I_{cp-i}}{I_{cp-p}} \right) \left( \frac{C_p}{C_i} \right) \left( \frac{g_{mi}}{T_{update} g_{mp}} \right)$$


$$\zeta = \frac{1}{2} \left( \frac{\omega_n}{\omega_z} \right) = \frac{1}{2} \sqrt{\frac{K_{ico} C_i}{2\pi M I_{cp-i} g_{mi}}} \left( \frac{I_{cp-p} T_{update} g_{mp}}{C_p} \right)$$

# ICO Control Waveforms

Standard Charge Pump PLL

 

PLL w/ Sample-Reset Filter

 

- PLL w/ sample-reset filter has dramatically reduced ripple voltage on oscillator control signal
- The control signal displays an almost ideal stair-step response

# Next Time

---

- VCOs